



LSC RFPD Analysis

1


OBSERVED INSTABILITIES IN RF OPAMPS

R. ABBOTT, 30 JULY 2010

Test Setup

2

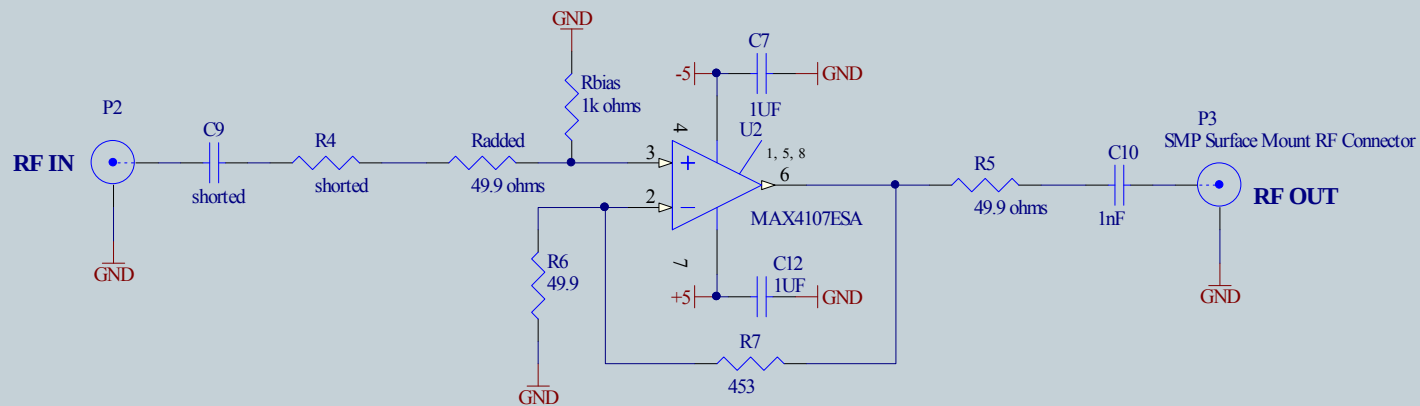
- Network Analyzer input on P2 with path shorted to U2. P3 terminated in 50 ohms. Measurement taken of input impedance (S11) vs. frequency



Observations of Input Impedance


3

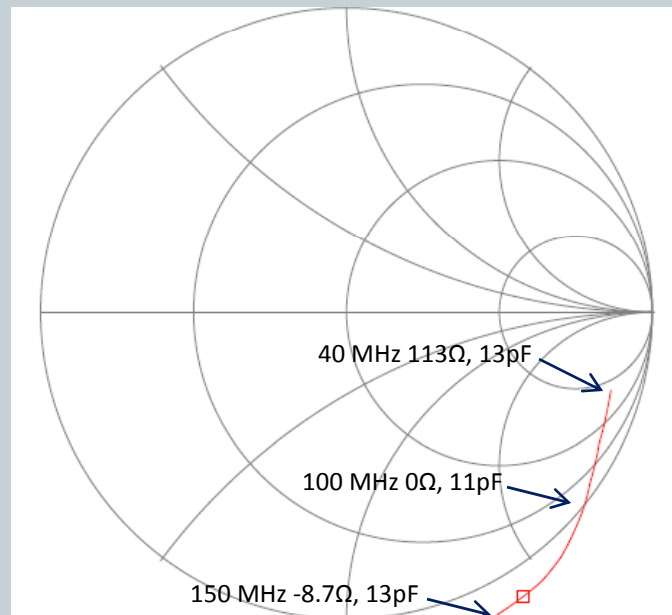- Frequencies above 100 MHz are potentially unstable (negative resistance)



Making A Negative Resistance

4

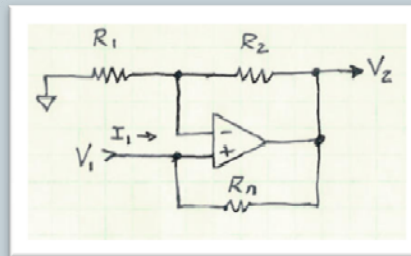

Opamp Circuit

Input Impedance

$$V_2 = \left(1 + \frac{R_2}{R_1}\right) V_1$$

$$I_1 = \frac{(V_1 - V_2)}{R_n} = -V_1 \frac{R_2}{R_n R_1}$$



$$R_{in} = \frac{V_1}{I_1} = -R_n \left(\frac{R_1}{R_2}\right) \quad \text{THE PRESENCE OF } R_n \text{ MAKES } R_{in} \text{ NEGATIVE}$$

A negative resistance implies gain. Gain in conjunction with a frequency selective network can, and does, create an oscillator.

Who Is To Blame?

5

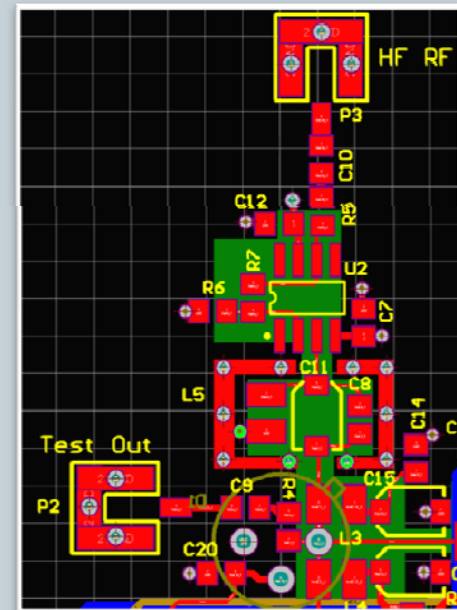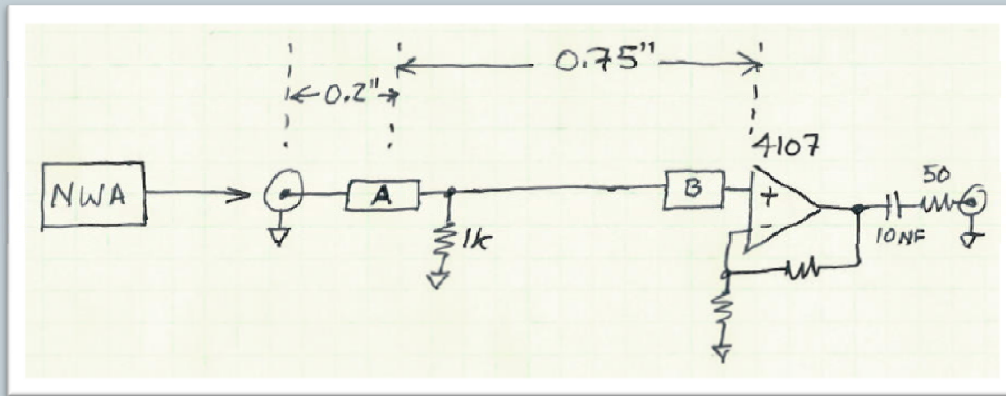- Positive feedback could be internal to the RF opamp, bleeding back out the + pin.
- Positive feedback could be related to circuit layout.



Measured Data

6

- Real and imaginary data in ohms
- A substantial change in input impedance is only seen when 50 Ω is added to the RF input, not the input of the opamp.
- Conclusion is that the phenomenon is related to layout.

Frequency	S11 Bare Board	S11 50 Ω on RF input	S11 50 Ω touching 4107
50 MHz	69.7 Ω , -258 Ω	103 Ω , -257 Ω	71 Ω , -257 Ω
100 MHz	0.4 Ω , -141 Ω	34 Ω , -132 Ω	1 Ω , -137 Ω
150 MHz	-8.2 Ω , -79 Ω	27 Ω , -80 Ω	-3 Ω , -73 Ω